

# HW #1: 32-bit ALU Design



國立陽明交通大學  
NATIONAL YANG MING CHIAO TUNG UNIVERSITY

Chun-Jen Tsai  
NYCU  
02/29/2024

# HW 1: Design a 32-bit ALU

---

- ❑ Goal: design an ALU module using Verilog.
  - An Arithmetic and Logic Unit (ALU) is the circuit module of a CPU that performs calculations on registers
  - This ALU will become part of a mini processor for future HW
  - Verilator and GTKWave will be used as logic simulation tools
  
- ❑ The deadline of the HW is on 3/14, by 5:00pm.

# The Port Definition of the ALU

- ❑ The ALU module is a combinational circuit with the I/O ports defined as follows:

```
module alu #(parameter DWIDTH = 32)
(
    input  [3 : 0]      op,      // Operation to perform.
    input  [DWIDTH-1 : 0] rs1,   // Input data #1.
    input  [DWIDTH-1 : 0] rs2,   // Input data #2.

    output [DWIDTH-1 : 0] rd,     // Result of computation.
    output zero,                 // zero = 1 if rd is 0, 0 otherwise.
    output overflow              // overflow = 1 if overflow happens.
);
```

- `op` triggers one of the six operations shown in the next slide
- All output signals shall be set to 0 if `op` is an invalid bit pattern

# Operation Table of the ALU

- ❑ You must implement 6 operations in the ALU

ALU operation	Function	op
and	$rd \leftarrow rs1 \text{ and } rs2$	0000
or	$rd \leftarrow rs1 \text{ or } rs2$	0001
add	Signed addition: $rd \leftarrow rs1 + rs2$	0010
sub	Singed subtraction: $rd \leftarrow rs1 - rs2$	0110
nor	$rd \leftarrow \sim(rs1 \text{ or } rs2)$	1100
slt	$rd \leftarrow (rs1 < rs2)? 32'h1 : 32'h0;$	0111

- Any input bit patterns to the port `op` not listed in the table will be considered invalid.

# Coding Comments

- ❑ You don't have to implement the 32-bit adder and subtractor at gate-level. You can simply use the Verilog operators `+` and `-` to do the job
- ❑ For the implementation of the `overflow` flag, please refer to section 3.2 of the textbook
  - Note that integers are represented in 2's complement here
  - Overflow conditions for additions and subtractions:

Operation	Operand A	Operand B	Result indicating overflow
$A + B$	$\geq 0$	$\geq 0$	$< 0$
$A + B$	$< 0$	$< 0$	$\geq 0$
$A - B$	$\geq 0$	$< 0$	$< 0$
$A - B$	$< 0$	$\geq 0$	$\geq 0$

# Guide to the Simulation Tools

---

- ❑ For this course, we will use Verilator as the waveform simulator and GTKWave as the waveform viewer for digital circuit designs
- ❑ A user's guide on how to install and get started with the tools under Linux or Windows Subsystem for Linux (WSL) is available in the following link:

<https://hackmd.io/SQHK4lmSR1-0b9V90srz5A>

- Note that the Verilator installed using the command:  
`$ sudo apt install verilator`  
under ubuntu may be too old, so you have to build your own Verilator from the source

# HW 1 Grading Guide

---

- ❑ You should upload your `alu.v` to E3 by the deadline
- ❑ The port declaration of your ALU module must follow the specification in this HW precisely
- ❑ A sample testbench, `HW1_tb.tgz`, is available on E3
  - Please read the `readme.txt` file in the package carefully
- ❑ For grading, TAs will use a more thorough testbench to test your design
  - Correctness of `rd` account for 70%
  - Correctness of `zero` and `overflow` account for 30%